

EE214 Lab-5 Report

Name: Medhansh

Roll No.: 25B3986

ALU

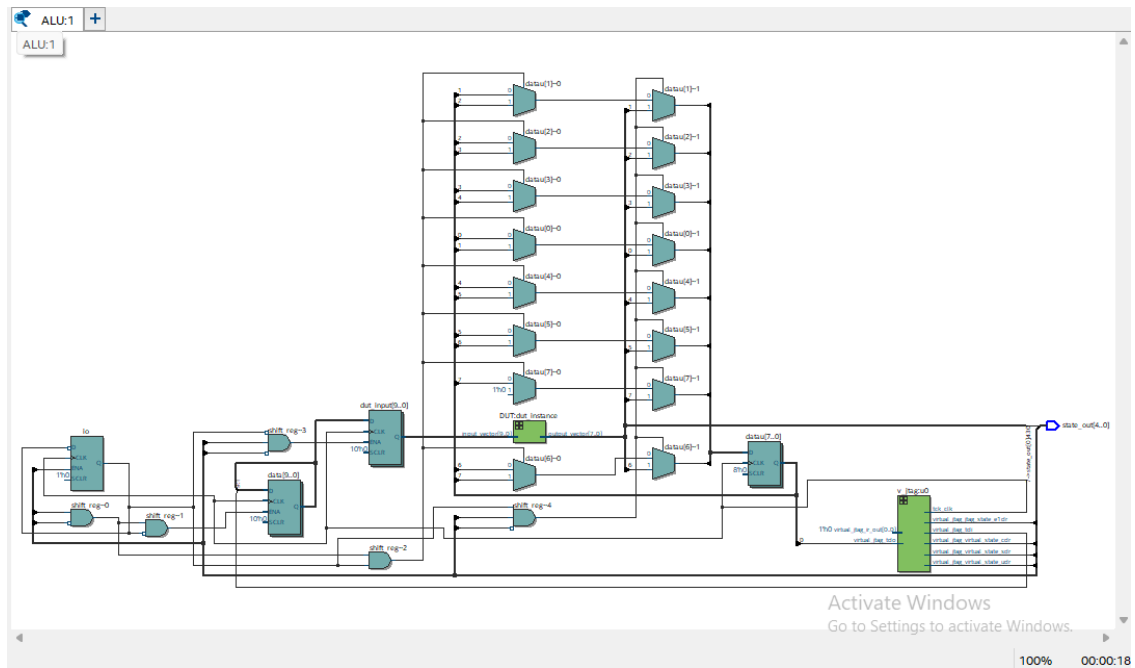


Figure 1: ALU schematic

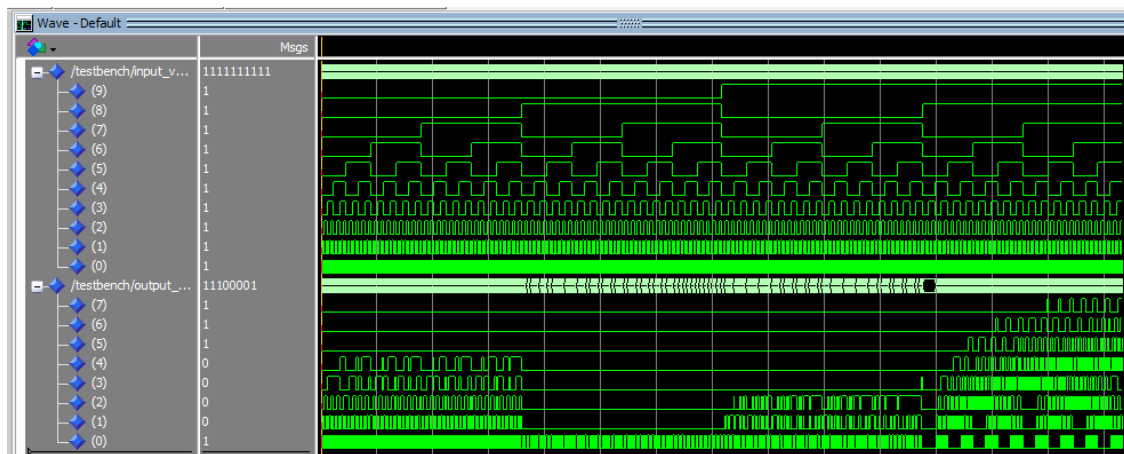


Figure 2: ALU simulation waveform


```

#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
# ** Note: SUCCESS, all tests passed.
#   Time: 14336 ns  Iteration: 0  Instance: /testbench

VSIM 2> ]

```

Figure 3: Transcript

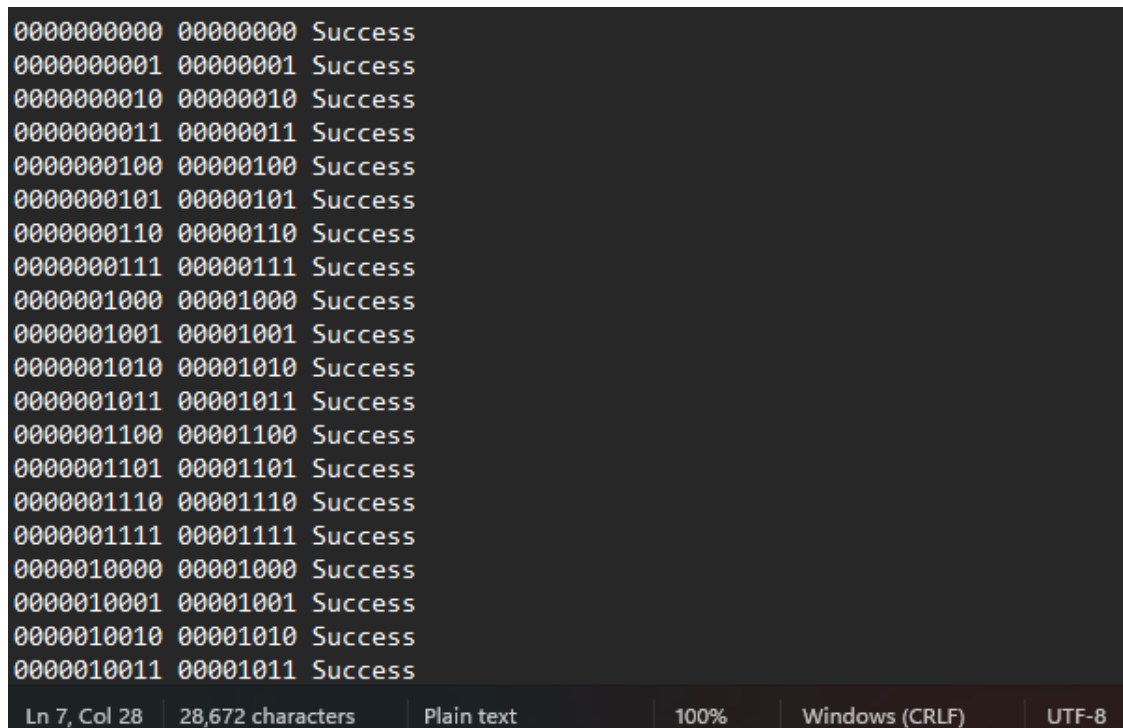

```

0000000000 00000000 Success
0000000001 00000001 Success
0000000010 00000010 Success
0000000011 00000011 Success
0000000100 00000100 Success
0000000101 00000101 Success
0000000110 00000110 Success
0000000111 00000111 Success
0000001000 00001000 Success
0000001001 00001001 Success
0000001010 00001010 Success
0000001011 00001011 Success
0000001100 00001100 Success
0000001101 00001101 Success
0000001110 00001110 Success
0000001111 00001111 Success
0000010000 00001000 Success
0000010001 00001001 Success
0000010010 00001010 Success
0000010011 00001011 Success

```

Ln 7, Col 28 | 28,672 characters | Plain text | 100% | Windows (CRLF) | UTF-8

Figure 4: Scanchain output file